

Digital System Assignment 1

- Full Adder & 4 Bit Adder Design-

Embedded Computer System Lab

Full Adder

Logic function – Sum

Truth Table


입 력			출 력
X	Y	Cin	Sum
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$\text{Sum} = \bar{X}\bar{Y}C_{in} + \bar{X}Y\bar{C}_{in} + X\bar{Y}\bar{C}_{in} + XYC_{in} \quad C_{out} = XY + XC_{in} + YC_{in}$$

$$= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\bar{X}\bar{Y} + XY)$$

$$= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\overline{\bar{X}Y + X\bar{Y}})$$
 
$$\text{Sum} = C_{in} \oplus (X \oplus Y)$$



Full Adder

Logic function – Carry Out

Truth Table

입 력			출 력
X	Y	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


$$\text{Sum} = \bar{X}\bar{Y}C_{in} + \bar{X}Y\bar{C}_{in} + X\bar{Y}\bar{C}_{in} + XYC_{in}$$

$$C_{out} = XY + XC_{in} + YC_{in}$$

$$= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\bar{X}\bar{Y} + XY)$$

$$= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\overline{\bar{X}\bar{Y} + XY})$$
 
$$\text{Sum} = C_{in} \oplus (X \oplus Y)$$



Design Assignment 1

■ Full Adder Design Source Code (Design Source)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Full_Adder is
    port (x, y, cin : in std_logic;
          sum : out std_logic;
          cout : out std_logic);
end Full_Adder;

architecture Behavioral of Full_Adder is
Begin
```

Complete the code here

```
end Behavioral;
```

Design Assignment 1

■ Full Adder Testbench Code (Simulation Source)

```
entity FA_TB is
end FA_TB;
```

```
architecture Behavioral of FA_TB is
```

```
  component Full_Adder port (
    x, y, cin : in std_logic;
    sum : out std_logic;
    cout : out std_logic);
  end component;
```

```
  signal X : std_logic := '0';
  signal Y : std_logic := '1';
  signal Cin : std_logic := '1';
  signal Sum, Cout : std_logic;
```

```
begin
```

```
  uut : Full_Adder port map (
    x=>X,
    y=>Y,
    cin=>Cin,
    sum=>Sum,
    cout=>Cout);
```

```
stim_proc : process
```

```
begin
```

```
  X <= '1';
```

```
  Y <= '1';
```

```
  wait for 10ns;
```

```
  Cin <= '0';
```

```
  wait for 10ns;
```

```
  X <= '0';
```

```
  Y <= '0';
```

```
  Cin <= '1';
```

```
  wait for 10ns;
```

```
  Cin <= '0';
```

```
  wait for 10ns;
```

```
  X <= '1';
```

```
  Y <= '0';
```


```
  wait for 10ns;
```

```
end process;
```

```
end Behavioral;
```

Design Assignment 1

■ Result

 


- X : 1, Y : 1, Cin : 1 → Sum : 1, Cout : 1
- X : 1, Y : 1, Cin : 0 → Sum : 0, Cout : 1
- X : 0, Y : 0, Cin : 1 → Sum : 1, Cout : 0

4 Bit Adder

■ Block Diagram

- 4개의 Full Adder가 직렬로 연결.

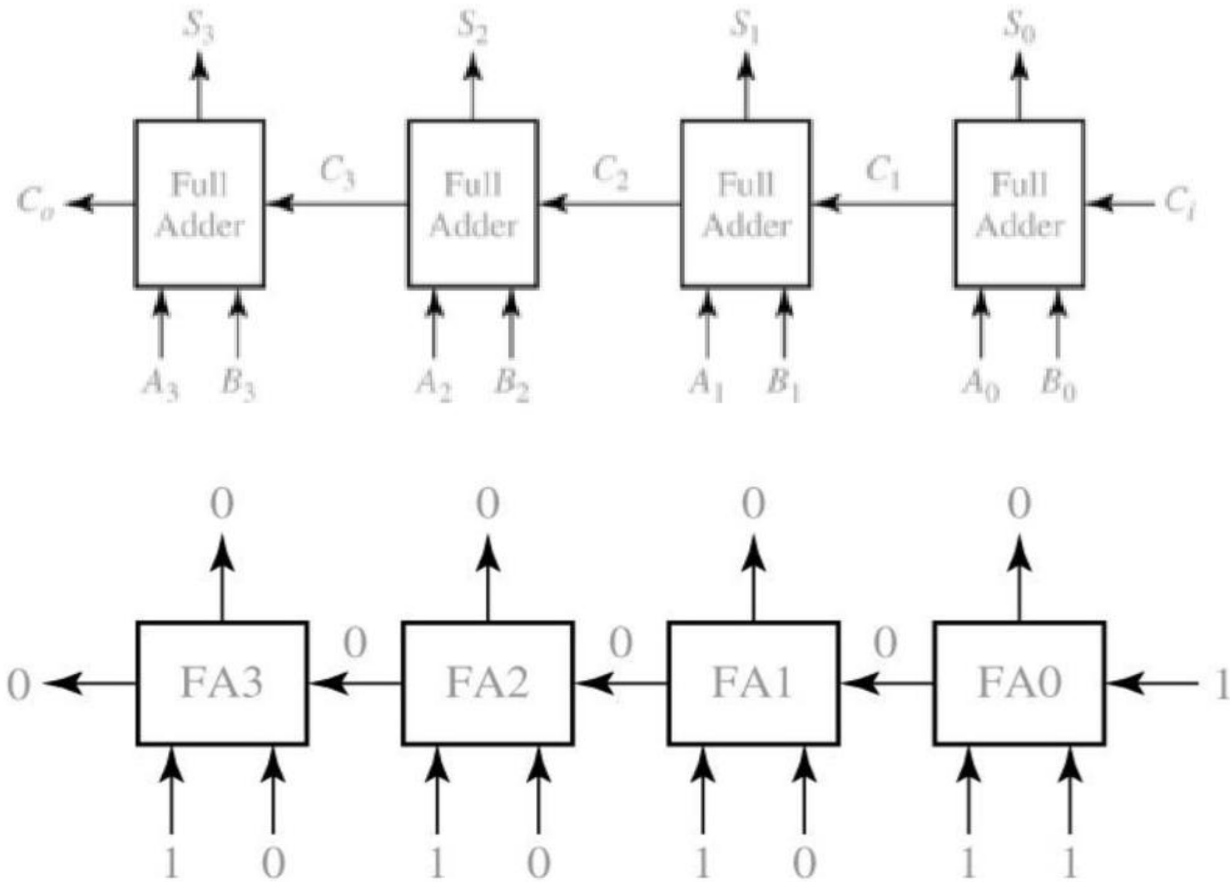

Design Assignment 2

■ 4 Bit Adder Design Source Code (Design Source)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Adder_4bit is
  port (x, y : in std_logic_vector(3 downto 0);
        cin : in std_logic;
        sum : out std_logic_vector(3 downto 0);
        cout : out std_logic);
end Adder_4bit;
```

architecture Behavioral of Adder_4bit is

Complete the code here

Begin

Complete the code here

end Behavioral;

Design Assignment 2

■ 4 Bit Adder Testbench Code (Simulation Source)

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Adder_4bit_TB is
end Adder_4bit_TB;

architecture Behavioral of Adder_4bit_TB is
    component Adder_4bit
        port (x, y : in std_logic_vector(3 downto 0);
              cin : in std_logic;
              sum : out std_logic_vector(3 downto 0);
              cout : out std_logic);
    end component;

    signal X : std_logic_vector(3 downto 0);
    signal Y : std_logic_vector(3 downto 0);
    signal Cin : std_logic;
    signal Sum : std_logic_vector(3 downto 0);
    signal Cout : std_logic;

begin
    uut : Adder_4bit port map (
        x=>X,
        y=>Y,
        cin=>Cin,
        sum=>Sum,
        cout=>Cout);

    stim_proc : process
        begin
            X <= "1111";
            Y <= "0001";
            Cin <= '1';
            wait for 10ns;

            Cin <= '0';
            wait for 10ns;

            X <= "0101";
            Y <= "1110";
            wait for 10ns;

            X <= "1100";
            Y <= "0111";
            Cin <= '1';
            wait for 10ns;


            X <= "1111";
            Y <= "1111";
            wait for 10ns;

            X <= "0110";
            Y <= "1001";
            Cin <= '0';
            wait for 10ns;
        end process;
end Behavioral;

```

Design Assignment 2


■ Result

 

- $X : f(1111) + Y : 1(0001) + Cin(1) = Cout(1) / Sum(0001)$
- $X : f(0101) + Y : e(1110) + Cin(0) = Cout(1) / Sum(0011)$
- 16진수로 되어 있어 결과 값을 한 눈에 이해하기 어려울 수 있음


Design Assignment 2

- Radix : unsigned decimal

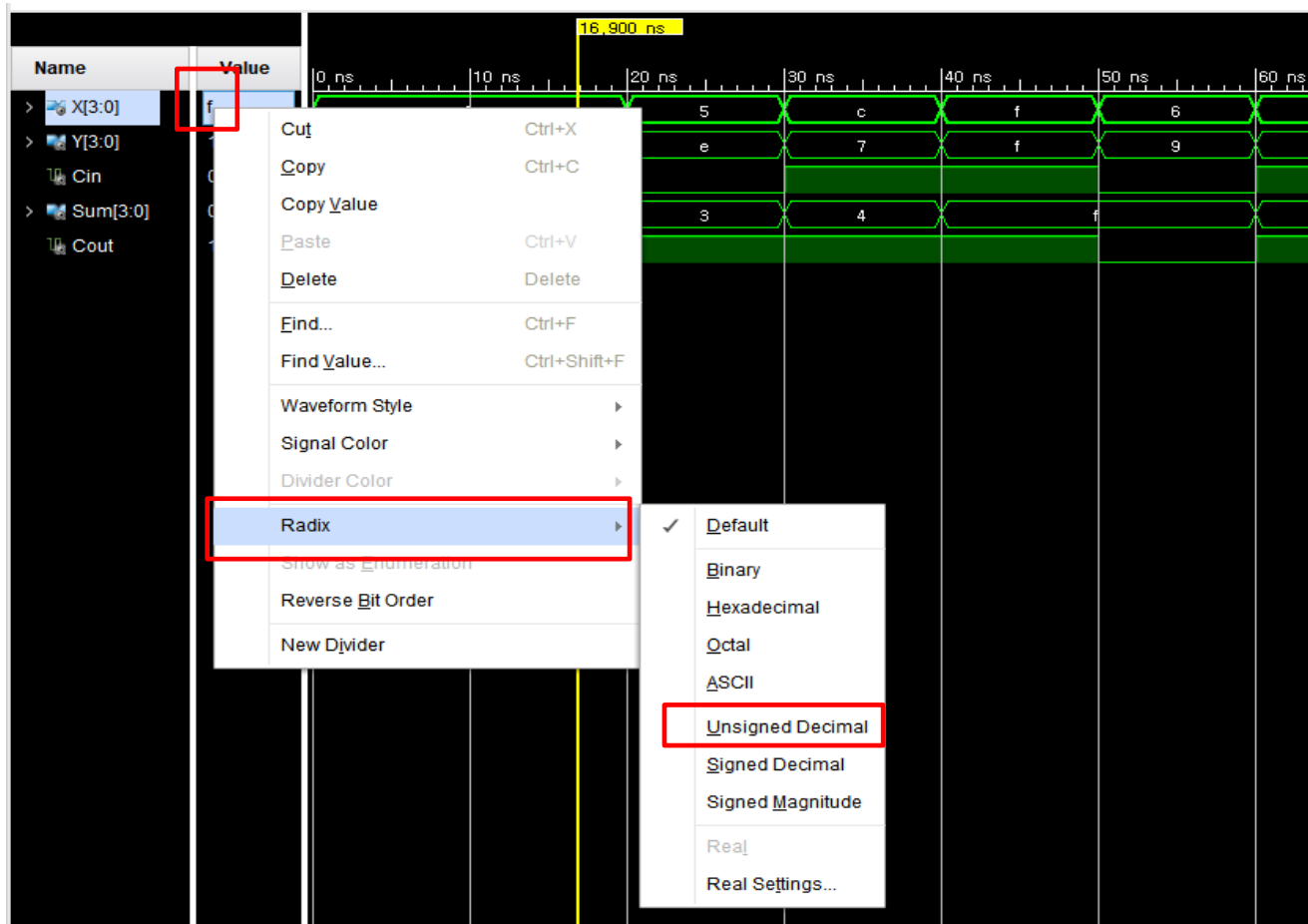

Design Assignment 2

■ Result

 

- $X : 15(1111) + Y : 1(0001) + \text{Cin} (1) = \text{Cout}(1) / \text{Sum} : 1(0001)$
- $X : 5(0101) + Y : 14(1110) + \text{Cin} (0) = \text{Cout}(1) / \text{Sum} : 3(0011)$

Submission

■ 제출

- i-campus에 파일 업로드 (보고서 + 소스코드를 하나로 압축해 제출)
- 압축된 파일명 : **학번_이름_HW1.xxx**
- Late Penalty
 - ❖ 1s ~ 1 day : -10%
 - ❖ 1day ~ 2day : -30%
 - ❖ 2day ~ 3day : -50%
 - ❖ 3day ~ : Cannot submit
- 문의사항 : 조교 고준성(myun243@skku.edu)

Submission

■ 제출 유의사항 (미흡시 불이익)

- 워드 프로그램에 설계한 VHDL 코드와 waveform을 첨부한 보고서
 - ❖ 설계한 VHDL 코드와 설명
 - 설계의 핵심이 되는 내용은 반드시 보고서에 설명
 - 설계한 방법과 이를 바탕으로 한 Adder 동작 원리 상세히 설명
 - TestBench 결과에만 맞게 설계 방향을 틀어서 진행한 경우, 대량 감점
TestBench 이외의 추가 경우의 수로 시뮬레이션 진행
 - ❖ 주어진 TB를 이용한 시뮬레이션 결과 waveform과 설명 및 분석
 - ❖ 보고서 파일명 : **학번_이름_HW1.xxx**
- 직접 작성한 VHDL 소스코드 파일 제출
 - ❖ Source code 파일명 : **학번_이름_FA.vhd / 학번_이름_4_Bit_Adder.vhd**
 - ❖ Testbench code 파일명 : **학번_이름_FA_tb.vhd / 학번_이름_4_Bit_Adder_tb.vhd**
 - ❖ 소스코드의 핵심 내용은 반드시 주석으로 설명할 것
- 보고서와 소스코드 파일을 하나로 압축해 제출